

$$i(t) = \frac{dq}{dt}$$

$$q_{\text{total}}(t) = \int_{t_0}^t i(t) dt$$

$$\overset{i(t)}{\longrightarrow} = \overset{-i(t)}{\longleftarrow}$$


$$V_{ab} = V_a - V_b = -V_{ba}$$

Voltage

Power


$$P = VI$$

Passive sign conv.

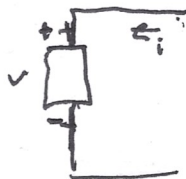

Passive Device (Load)
Consumes power


active sign conv.

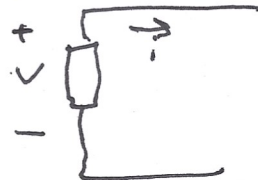


Active Element (Source)
Delivers Power

Sources

Independent Sources - Not dep on circuit

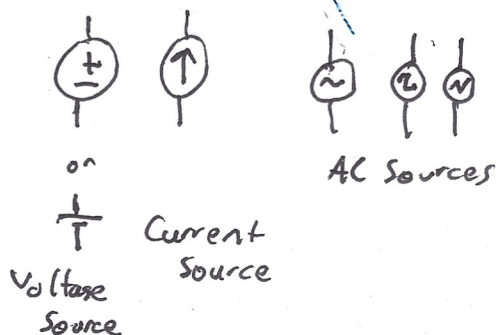

Dependent Sources - Dep on Circuit

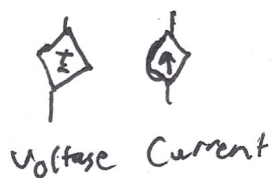

VCVS - V controlled V source
CCVS - I contr. V source.
VCCS - V contr. I source
CCCS - I contr. I source

Circuits

Open



Short



Turn off sources

= Short V, Open I

Series



Parallel



Ohm's Law

$$v(t) = i(t) R \quad \text{or} \quad i(t) = \frac{v(t)}{R}$$

Resistors

$$R = \rho \frac{L}{A} \quad \rho = \text{resistivity}$$

$$G = \frac{1}{R} \quad (\text{Conductance})$$

Power from R

$$P = vi \Rightarrow P = \frac{v^2}{R} \quad \text{or} \quad P = i^2 R$$

Kirchoff's Laws

KCL: Sum of all currents leaving a node = 0

$$\sum i_n(t) = 0$$

Series
 $R_{eq} = \sum R_n$



Parallel
 $R_{eq} = \left(\sum \frac{1}{R_n} \right)^{-1}$

(Parallel)


$$i_n(t) = \frac{R_{eq}}{R_n} i(t)$$

aka

$$i_1(t) = \frac{R_2}{R_1 + R_2} i(t)$$

or

$$i_2(t) = \frac{R_1}{R_1 + R_2} i(t)$$

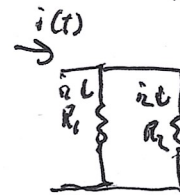

KVL: Sum of voltages around a closed path = 0

$$\sum v_n(t) = 0$$

Equivalent Resistance

Turn off indep sources + Calc Req. (if nodes)

If dep sources, Use test voltage/current
 (jntest) Calc other value

$$R_{eq} = \frac{V}{I}$$

(Series)

$$V_n(t) = \frac{R_n}{R_{eq}} v(t)$$

aka

$$v_1(t) = \frac{R_1}{R_1 + R_2} v(t)$$

or

$$v_2(t) = \frac{R_2}{R_1 + R_2} v(t)$$



$$I_n(t) = \frac{R_{eq}}{R_n} i(t)$$

Nodal Analysis



1. Number all essential nodes
2. Write KCL eqs for all nodes. Replace any ^{unknown} current w/ Nodal Voltages. (Ohm's Law)
3. $G\vec{V} = \vec{I}$ (Group Eqs into Matrix)
4. Solve using $\vec{V} = G^{-1}\vec{I}$ (G bc most coeffs will be $\frac{1}{R}$ vals)
5. Calc. needed vals from nodal voltages

Mesh Analysis

1. List all Mesh Currents w/ direction
2. Write KVL eqs for all meshes. Replace any ^{unknown} voltage w/ Mesh Currents. (Ohm's Law). Remember to write multiple mesh currents if mult. flow through the component.
3. $R\vec{I} = \vec{V}$ (Group Eqs into Matrix)
4. Solve using $\vec{I} = R^{-1}\vec{V}$ (R bc most coeffs will be R)
5. Calc needed vals from mesh currents

Basic Principles

Linearity - Scales Linearly

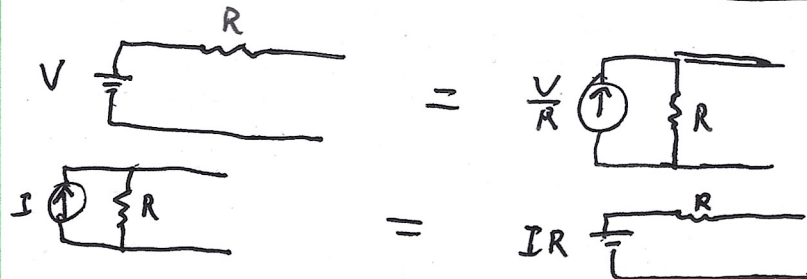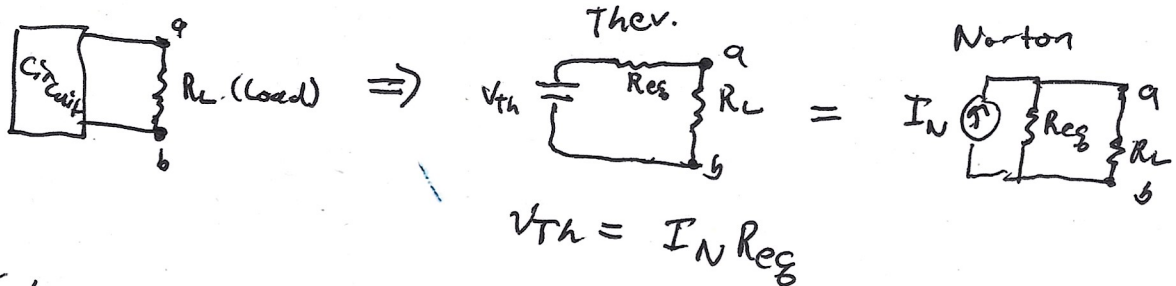Superposition - Check one indep
Source at a time,
add up effectsSource TransformationNorton / TheveninCalc R_{eq} , as prev writtenCalc V_{th} by a open circuit (on R_L) use KCL/KVLCalc I_N by a short circuit (on R_L)~~Add a resistor~~

Capacitor

$$q = CV \quad \text{- based on Voltage} \quad C = \frac{\epsilon A}{d} \quad \text{- based on geometry}$$

$$i_C(t) = C \frac{dV_C}{dt}$$

Voltage Across a Capacitor is ~~Continuous~~

- Capacitor behaves as an open circuit ~~in~~ in DC stable state circuits and as a short immediately after connection.

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(x) dx \Rightarrow V_C(t) = \frac{1}{C} \int_{t_0}^t i_C(x) dx + V_C(t_0)$$

$$P_C(t) = V_C(t) i_C(t) \Rightarrow W_C(t) = \frac{1}{2} C V_C^2(t)$$

Power Energy

$$\frac{1}{C_{eq}} = \sum \frac{1}{C_i} \quad \text{- Voltage is distr. by ratio of capacitances}$$

Series

$$C_{eq} = \sum C_i \quad \text{- voltage across each } C \text{ is } =$$

parallel

Inductors

$$L = \mu_0 \frac{N^2}{l} S \quad \text{- based on geometry}$$

(N turns, l length)
(S surface Area)

$$V_L(t) = L \frac{di_L(t)}{dt}$$

Current through an Inductor is Continuous

- Inductor behaves as a short circuit in DC stable state circuits.

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t V_L(x) dx \Rightarrow i_L(t) = \frac{1}{L} \int_{t_0}^t V_L(x) dx + i_L(t_0)$$

$$P_L(t) = V_L(t) i_L(t) \Rightarrow W_L(t) = \frac{1}{2} L i_L^2(t)$$

Power

$$L_{eq} = \sum L_i$$

Series

$$\frac{1}{L_{eq}} = \sum \frac{1}{L_i}$$

parallel

RC Circuits

$$V_c(t) = V_{cc} + (V_c(t_0) - V_{cc})e^{-\frac{(t-t_0)}{\tau}} \quad \tau = RC$$

$$t = \tau : 63.2\%, \quad t = 3\tau : 95\% \quad t = 5\tau : 99.3\%$$

$$V_{cc} = V_c(\infty)$$

RL Circuits

$$i_L(t) = \frac{V_{cc}}{R} + (i_L(t_0) - \frac{V_{cc}}{R})e^{-\frac{(t-t_0)}{\tau}} \quad \tau = \frac{L}{R}$$

$$t = \tau : 63.2\% \quad t = 3\tau : 95\% \quad t = 5\tau : 99.3\%$$

$$i_L(\infty) = \frac{V_{cc}}{R}$$

Basic Sinwave

$$v(t) = V_m \sin(\omega t + \phi)$$

V_m - Amplitude

ω - radian freq.

ϕ - phase shift

$$f = \frac{1}{T} = \frac{\omega}{2\pi} \text{ freq.}$$

T - Time period

Complex nums

$$X = a + jb \Rightarrow X = r \angle \theta = r e^{j\theta}$$

$$\underline{-\pi < \theta < \pi}$$

$$r = \sqrt{R(x)^2 + I(x)^2}, \theta = \tan^{-1} \left(\frac{I(x)}{R(x)} \right)$$

$$r = \sqrt{a^2 + b^2}, \theta = \tan^{-1} \left(\frac{b}{a} \right)$$

$$X = r_1 \angle \theta_1$$

$$Y = r_2 \angle \theta_2 = \cancel{r_1 r_2 \angle \theta_1 + \theta_2}$$

$$XY = r_1 r_2 \angle \theta_1 + \theta_2 \quad \frac{X}{Y} = \frac{r_1}{r_2} \angle \theta_1 - \theta_2$$

$$\frac{1}{X} = \frac{1}{r_1} \angle -\theta_1 \quad X^n = r_1^n \angle n\theta$$

$$X^* = r_1 \angle -\theta_1 \quad j = 1 \angle 90^\circ$$

Phasors

$$x(t) = A \cos(\omega t + \theta^\circ) \Rightarrow \tilde{X} = A \angle \theta$$

Impedance

$$\tilde{V} = Z \tilde{I}$$

$$\text{Admittance} \Rightarrow Y = \frac{1}{Z}$$

$$Z_R = R \quad Z_C = \frac{1}{j\omega C} \quad Z_L = j\omega L$$

$$= -\frac{j}{\omega C}$$

Power

$$p(t) = v(t) i(t) \quad \Rightarrow \quad \text{Instantaneous Power}$$

$$p(t) = \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

Average Power

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \quad \Rightarrow \quad P = R \left(\frac{1}{2} \vec{V} \vec{I}^* \right)$$

$$= V_{rms} I_{rms} \cos(\theta_v - \theta_i) \quad \begin{aligned} V_{eff} &= V_{rms} = V_m / \sqrt{2} \\ I_{eff} &= I_{rms} = I_m / \sqrt{2} \end{aligned}$$

$$X_{eff} = X_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} x^2(t) dt}$$

Max abs pow

$$P_{load(max)} = \frac{|V_{th}|^2}{8 R_{eq}}$$

$$\Downarrow$$

$$\Downarrow$$

$$Z_{load} = Z_{eq}^*, \quad R_{load} = R_{eq}, \quad X_{load} = -X_{eq}$$

Inductance

• Self-Inductance - $L = \frac{\Phi}{I}$

$$\Phi_{12} = \int_{S_2} \vec{B}_1 \cdot d\vec{S}_2$$





• Mutual-Inductance - $L_{12} = \frac{N_2 \Phi_{12}}{I_1}$ ($N_2 = \# \text{ of turns}$) (Loop 1
+
Loop 2)

• $L_{11} > L_{12}$ bc $\Phi_{11} > \Phi_{12} \Rightarrow L_{12} = L_{21}$



• $V_{L1} = L_{12} \frac{di_2(t)}{dt}$



$V_{L2} = L_{12} \frac{di_2(t)}{dt}$

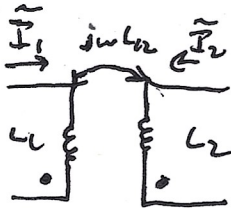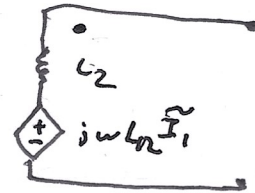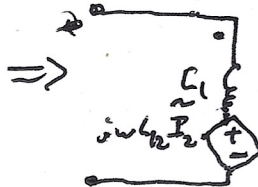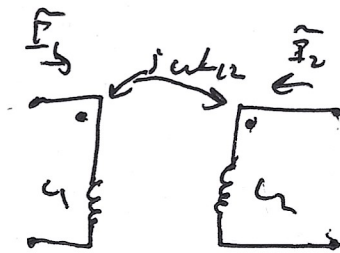Mutual Inductance

$\Rightarrow$

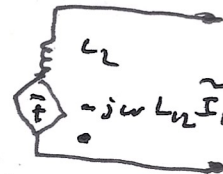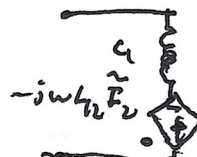


Power
 $P(t_1 < t < t_2) = P_2(t) = i_1(t) L_{12} \frac{di_2(t)}{dt} + i_2(t) L_{21} \frac{di_1(t)}{dt}$

$P(0 < t < t_1) = P_1(t) = i_1(t) L_1 \frac{di_1(t)}{dt}$

$w(t_1 < t < t_2) = L_{12} i_1(t_1) i_2(t_2) + L_{21} L_2 i_2^2(t_2)$

$w_T = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm L_{12} i_1 i_2$ (+ if same side dot)

• Coupling Coeff - $k = \frac{L_{12}}{\sqrt{L_1 L_2}}$

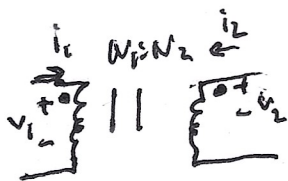Transformer



$\Rightarrow \frac{v_2(t)}{v_1(t)} = \frac{N_2}{N_1} \Rightarrow n = \frac{N_2}{N_1}$


$\frac{i_2(t)}{i_1(t)} = -\frac{1}{n}$

(Opp dots)

$\frac{v_2(t)}{v_1(t)} = -n$

$\frac{i_2(t)}{i_1(t)} = \frac{1}{n}$

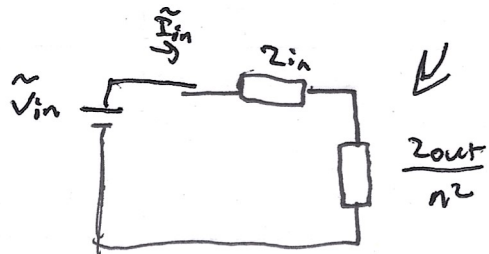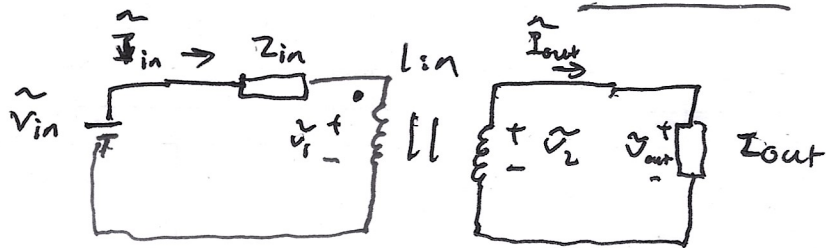Transformer Control

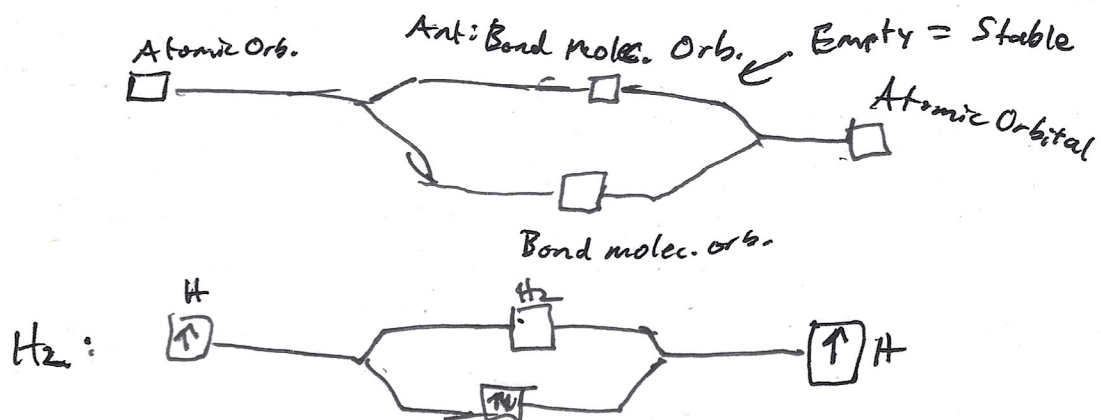Molecular Orbitals

For each orbital one of these exists (p, s etc.)

Silicon Crystal

Anti bond → conduction band
Bond → valence band.

Si = 4 valence



Band Gap → Ins = big Semi = small Conduc = overlap

Doping

(n) Donors N, P, As, Sb, Bi

(p) Acceptors B, Al, ~~Ge~~ Ga, In, Tl

Undoped semi = intrinsic semi conductor ⇒ $n = p = n_i$ (intrinsic carrier density)

n - elec conc.

p - hole conc.

$$n \approx N_D$$

$$p \approx N_A$$

Doping concentrations



$$np = n_i^2$$

(n) $p \approx \frac{n_i^2}{N_D}$ for $N_D \gg n_i, N_D \gg N_A$

(p) $n \approx \frac{n_i^2}{N_A}$ for $N_A \gg n_i, N_A \gg N_D$

Pn junction = semi trans. from p to n type
pn junction

idealized:

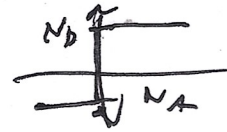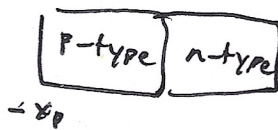

$$N_D^+ = N_D \text{ (ionized)}$$

$$N_A^- = N_A$$

$$\rho = q(p-n + N_D - N_A)$$

Charge dens.

$$V(f) - V(i) = - \int_i^f E_x dx$$

$$E_x(x) = \int_{-x_p}^x \frac{\rho}{\epsilon_r \epsilon_0} dx$$

$\epsilon_r = \text{perm. of}$
 semi

$$\epsilon_0 = 8.854 \cdot 10^{-12}$$

$$V_{bi} = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

Depletion width

$$q N_A V_p = q N_D V_n$$

$$V_p = x_p A, V_n = x_n A$$


$\Downarrow$

$$q N_A x_p = q N_D x_n \Rightarrow$$

$$x_n = \frac{N_A}{N_D} x_p$$

Diodes

Easy current flow in 1 direction.

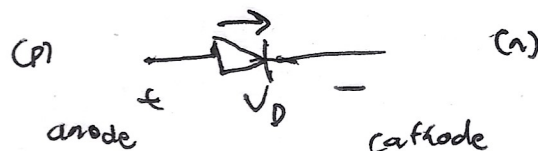


$$I = I_0 (e^{(qV_A/kT)} - 1)$$

q - electron charge

k - boltzman const.

T - temperature

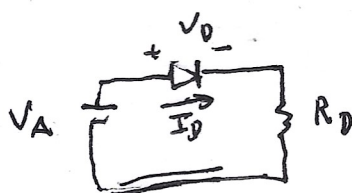 I_0 - reverse bias sat. current $kT/q \approx 0.0259$ (thermal volt. at 300K)Simple Diode Circuit

$$V_A = V_D + I_D R_D \Rightarrow V_A = V_D + I_0 (e^{qV_D/kT} - 1) R_D$$

Two methods: Graph/Numeric

Graph: $\frac{V_A - V_D}{R}$ vs V_D and $I_0 (e^{qV_D/kT} - 1)$ vs V_D (x, y) intersection is (V_{DQ}, I_{DQ}) Numeric: Calc: $I_D = \frac{V_A - V_D}{R_D}$ (Assume $V_D \approx 0$)

$$V_D = \frac{kT}{q} \ln \left(\frac{I_D}{I_0} + 1 \right)$$

Repeat these two until precision reached.


Simplified Diode Model
 $i_D = 0 \Rightarrow$ Diode (reverse bias)
 $v_D < 0$ is open circuit

 $i_D > 0 \Rightarrow$ Diode (forward bias)
 $v_D \approx 0$ is a short circuit
Guess one & check: (reverse: $0 > I$, forward: $0 < I$) $0.5 < V_D < 0.9$ usual,approx. $V_D = 0.7$ V usually.~~Diode model~~~~Diode model~~~~Diode has least resistance in parallel will be on.~~ $V_{th} \approx V_{min}$ $V_{th} = 0.7$ approx


How to solve

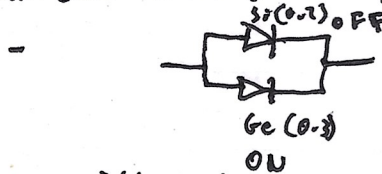
1. Assume $V_D = 0.7$ (Si), $V_D = 0.3$ (Ge) (Ideal is 0, but not feasible)
2. Make assumptions abt forward/reverse bias
3. Solve the circuit wr the assumptions.
4. Verify assumptions.

- Current will flow path of least Resistance / Higher Voltage wins




- with resistors both can be on.

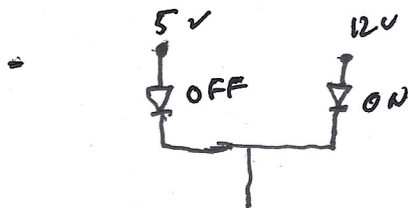

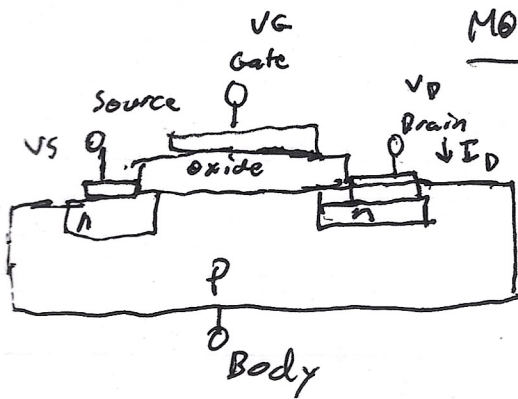MOSFET Transistors

n-channel mosfet
charge carrier = electrons

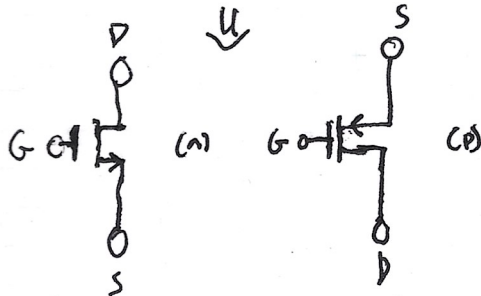p-channel Mosfet switches p+n
and uses holes as charge carrier
making them hotter,



Current Goes $D \rightarrow S$ in n,
 $S \rightarrow D$ in p.

V_t = Threshold voltage for V_G

about n type (p same but v's) ($I_D = 0$ if $V_G \leq V_t$) OFF switch

V_{Dsat} = Saturation Voltage

$V_D \ll V_{Dsat}$ - Linear I_D increase

$V_D < V_{Dsat}$ - Logarithmic I_D increase till V_{Dsat}

$V_D > V_{Dsat}$ - constant I_D

$$V_{Dsat} = V_G - V_t$$

$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

Transconductance parameter (based on construction)

$$k = \mu_n C_{ox} \left(\frac{W}{L} \right)$$

$$I_D = k(V_{GS} - V_t)V_{DS} - \frac{1}{2}kV_{DS}^2$$

$$I_D = \frac{k}{2}(V_{GS} - V_t)^2$$

$$V_{GS} \leq V_{GS} - V_t$$

$$V_{DS} \leq V_G - V_t$$

$$V_{DS} \geq V_{GS} - V_t$$

$$V_D \geq V_G - V_t$$

Triode region

Saturation region

Triode/Sat. Boundary is at $V_{DS} = V_{GS} - V_t$

$$I_D = \frac{k}{2} V_{Dsat}^2 \text{ @ transition.}$$

V_{G1A} - cutoff $\rightarrow$ sat

V_{G1B} - sat $\rightarrow$ triode

$$I_D = 0 \text{ for } V_G \leq V_t$$

can be used for amps / logic gates. $\Rightarrow$

(controlled by V_G (tags))

$$I_G = 0, I_D = I_S$$

Triode $\Rightarrow$ ~~logic on~~ AND

Cutoff $\Rightarrow$ Logic OFF

Saturation $\Rightarrow$ ~~logic on~~

Mos + transistors

specify k and V_t